

PY111 Practice Midterm 2 SOLUTIONS

NAME:

LAST FOUR DIGITS OF SSN:

Answer in the space provided. You may use the backs of sheets if required. Box your answers on questions 2 and 3. There are 30 possible points in this midterm.

written response

1. Does it make sense to separate the world into conductors and insulators?

No. There is really a continuum of materials in terms of conductivity. And it is even more complicated if you consider semiconductors...

partial credit questions

2. An electron is accelerated from rest through a potential of 10,000 V and sent down a long evacuated tube which has a target of charge $-6 \mu\text{C}$ at the end. Determine how close the electron gets to the target.

Conserve energy to solve this problem. The initial EPE is given by qV where $V = 10000$. The initial KE is zero. The sum of these must equal the final KE, which is zero, and the final EPE, which we approximate to be $EPE_f = qV = kqQ/R$ where Q is $6 \mu\text{C}$ and R is the distance of closest approach. Solving (q cancels out) gives $R = 5.4\text{m}$.

3. An electric field does 5.8 mJ of work in moving a charge with $q = +3\mu\text{C}$ from A to B.

(a) What is the value of $EPE_A - EPE_B$?

(b) Determine $V_A - V_B$.

(c) Is A or B at higher potential?


(a) $EPE_A - EPE_B = W_{AB} = 5.8\text{mJ}$.

(b) $V_A - V_B = (EPE_A - EPE_B)/q \approx 2\text{kV}$

(c) Since the field does work on the charge, the charge must be moving it to lower potential, $V_B < V_A$.

multiple choice questions

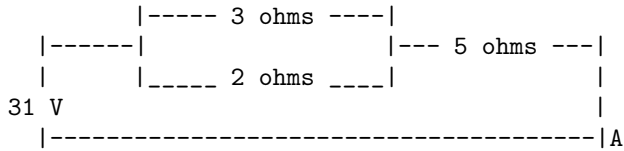
4. Determine the current through the 2 ohm resistor.



- (a) 2 A
(b) 3 A
 (c) 1 A
 (d) 4 A

$R_{eq} = 2 \cdot 3 / (2 + 3) + 5 = 31/5$ ohms. Thus $I = 5A$. Thus the voltage drop across the 3 and 2 ohm portion of the circuit is 6V and the current through the 2 ohm resistor is 3A.

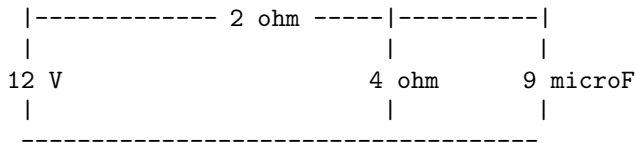5. Determine the charge on the capacitor after it has fully charged.



- (a) 36 μC
(b) 72 μC
 (c) 18 μC
 (d) 180 μC

Once the capacitor is fully charged no current flows through it. Thus the total current is $I = 2A$. Since $q = CV$ and the voltage drop across the capacitor (and 4 ohm resistor) is 8V, we get $q = 72 \cdot 10^{-6}C$.

6. A cardiologist doubles the length of a copper wire feeding artificial heart, what happens to the wire's resistance?

- (a) halves
 (b) stays the same
(c) doubles
 (d) quadruples
 Use $R = \rho L/A$

7. An electric space heater has been brought into the ER in an attempt to keep patients from freezing. If it is made of wire with a resistance on 12 ohms and is plugged into a 115V AC outlet, how much heat is added to the room in two minutes?

- (a) 8 kJ
 (b) 66 kJ
 (c) 2200 J
 (d) 1100 J
(e) 0.13 MJ

Use $P = V^2/R$ to get $P = 1100W$. Multiply by 120 seconds to get the total heat energy $Q = 1.3 \cdot 10^5 J$.

8. If a capacitor stores $5 \cdot 10^{-4}$ J of energy when attached to 10 V battery, how much does it store when attached to a 20 V battery?

- (a) 2 mJ**
 (b) 20 mJ
 (c) 1 mJ
 (d) 0.5 mJ

The voltage doubles and $E = 1/2CV^2$.

equations

$$\begin{aligned}
W_{AB} &= EPE_A - EPE_B & qV &= EPE & V &= kq/r \\
E &= -\frac{\Delta V}{\Delta s} & q &= CV & \kappa &= E_0/E & C &= \kappa\epsilon_0 A/d \\
E &= \frac{1}{2}CV^2 & E &= \frac{1}{2}\kappa\epsilon_0 E^2 & I &= \frac{\Delta q}{\Delta t} & V &= IR & R &= \rho L/A & P &= IV \\
\bar{P} &= I_{rms}V_{rms} & V &= V_0 \sin 2\pi ft & R_{eq} &= R_1 + R_2 + \dots & 1/R_{eq} &= 1/R_1 + 1/R_2 + \dots \\
C_{eq} &= C_1 + C_2 + \dots & 1/C_{eq} &= 1/C_1 + 1/C_2 + \dots & q &= q_0(1 - e^{-t/RC}) & q &= q_0 e^{-t/RC} \\
\epsilon_0 &= 8.85 \cdot 10^{-12} C^2/N \cdot m^2 & q_e &= -1.6 \cdot 10^{-19} C & m_e &= 9.1 \cdot 10^{-31} kg & k &= 8.99 \cdot 10^9 N \cdot m^2/C^2
\end{aligned}$$